



COMPILED & CIRCULATED BY
Dr. Tapanendu Kamilya
Assistant Professor, Department of Physics, Narajole Raj College

Topic:

Digital Circuits: X-OR & X-NOR Gates, 2's compliment, Subtraction by 2's compliment, Half Adder, Full Adder


Digital Circuits:

X-OR & X-NOR Gates:

XOR Gate (Exclusive OR) is a digital logic Gate that gives a true (1 or HIGH) output when the number of inputs is only odd.



... is equivalent to ...

 

$$A \oplus B = A\bar{B} + \bar{A}B$$

Truth Table:

A	B	XOR
0	0	0
0	1	1
1	0	1
1	1	0




COMPILED & CIRCULATED BY

Dr. Tapanendu Kamilya


Assistant Professor, Department of Physics, Narajole Raj College

X-NOR Gates:

 The XNOR gate (Exclusive NOR) is a digital logic gate whose function is the logical complement of the Exclusive OR (XOR) gate.



Symbol of X-NOR Gate

 

Construction of X-NOR Gate: $Y = AB + \overline{AB}$

Truth Table:

A	B	X-NOR $Y = AB + \overline{AB}$
0	0	1
0	1	0
1	0	0
1	1	1



COMPILED & CIRCULATED BY
Dr. Tapanendu Kamilya
Assistant Professor, Department of Physics, Narajole Raj College

1's complement of 111001 is 000110. Hence

$$\begin{array}{r} \text{Minued -} \quad \quad 101011 \\ \text{1's complement -} \quad +\underline{000110} \\ \hline \quad \quad \quad \quad \quad 110001 \text{ (No carry)} \end{array}$$

Hence the difference is - 1110 (Ans)

Subtraction using 2's Complement

These are the following steps to subtract two binary numbers using 2's complement

- In the first step, we have to find the 2's complement of the subtrahend.
- Then, we have to add the complement number with the minuend.
- After adding, if we get the carry by adding both the numbers, then we discard this carry and the result is positive else take 2's complement of the result which will be negative.

Example 1: Subtract: 10101 - 00111

We take 2's complement of subtrahend 00111, which is 11001. Now, sum them. So,

$$10101 + 11001 = \mathbf{1}01110$$

In the above result, we get the carry bit 1. So we discard this carry bit and remaining is the final result and a positive number.

Hence the difference is 01110 (Ans)

Example 2: Subtract: 10101 - 10111

We take 2's complement of subtrahend 10111, which comes out 01001. Now, we add both of the numbers. Hence,

$$10101 + 01001 = 11110$$

In the above result, we didn't get the carry bit. So calculate the 2's complement of the result, i.e., 00010. It is the negative number and the final answer.

Hence the difference is 00010 (Ans)




COMPILED & CIRCULATED BY

Dr. Tapanendu Kamilya


Assistant Professor, Department of Physics, Narajole Raj College

Half Adder

Half Adder is combinational logic circuit which sums two 1-bit digits. The half adder produces a sum of the two inputs. A half adder is used for adding together the two least significant digits in a binary sum. The half adder can add only two input bits (A and B) and has nothing to do with the carry if there is any in the input. That means the binary addition process is not complete and that's why it is called a half adder.

 

Symbol/Block Diagram of Half Adder

 

Circuit Diagram of Half Adder



COMPILED & CIRCULATED BY


Dr. Tapanendu Kamilya

Assistant Professor, Department of Physics, Narajole Raj College


Truth Table			
Input		Output	
A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

Truth Table of Half Adder

Full Adder

 

Symbol/Block Diagram of Full Adder

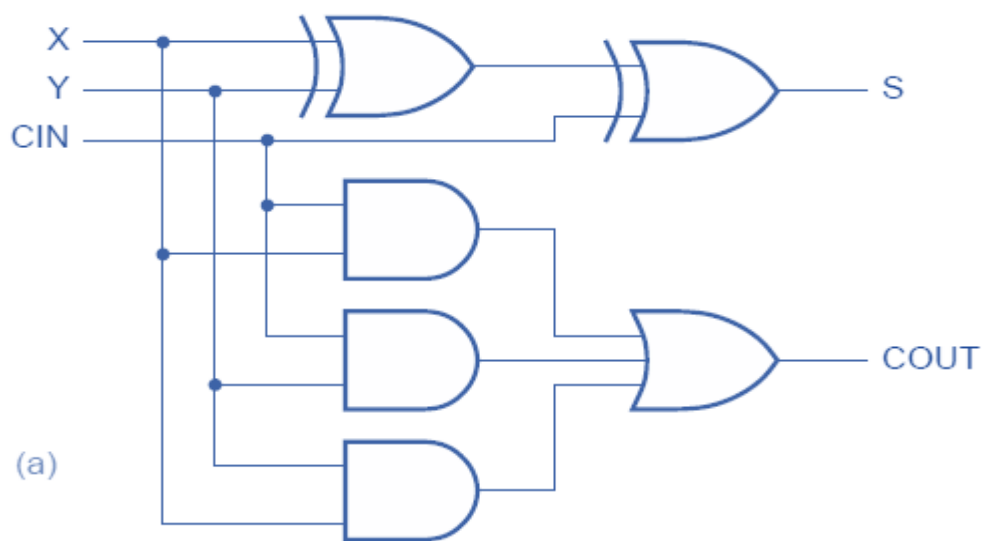

Circuit Diagram of Full Adder



COMPILED & CIRCULATED BY

Dr. Tapanendu Kamilya

Assistant Professor, Department of Physics, Narajole Raj College

Input			Output	
A	B	C _{in}	Sum	Carry
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Truth Table of Full Adder

A	B	C _{in}	SUM (S)	C _{out}
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1



AB \ C _{in}	\bar{C}_{in}	C _{in}
$\bar{A}\bar{B}$		
$\bar{A}B$		1
AB	1	1
$A\bar{B}$		1

AB \ C _{in}	\bar{C}_{in}	C _{in}
$\bar{A}\bar{B}$		1
$\bar{A}B$	1	
AB		1
$A\bar{B}$	1	

$$C_{out} = \bar{A}.B.C_{in} + A.\bar{B}.C_{in} + A.B.\bar{C}_{in} + A.B.C_{in} \quad S = \bar{A}.\bar{B}.C_{in} + \bar{A}.B.\bar{C}_{in} + A.\bar{B}.\bar{C}_{in} + A.B.C_{in}$$

K-Map for Full Adder



COMPILED & CIRCULATED BY

Dr. Tapanendu Kamilya


Assistant Professor, Department of Physics, Narajole Raj College

$$\begin{aligned}
 \text{Sum} &= \bar{A}\bar{B}C_{in} + \bar{A}B\bar{C}_{in} + A\bar{B}\bar{C}_{in} + ABC_{in} \\
 &= C_{in}(\bar{A}\bar{B} + AB) + \bar{C}_{in}(\bar{A}B + A\bar{B}) \\
 &= C_{in}(A \odot B) + \bar{C}_{in}(A \oplus B) \\
 &= C_{in}(\overline{A \oplus B}) + \bar{C}_{in}(A \oplus B) \\
 &= C_{in} \oplus (A \oplus B)
 \end{aligned}$$

$$\begin{aligned}
 \text{Carry} &= AB + AC_{in} + BC_{in} \\
 &= AB + AC_{in}(B + \bar{B}) + BC_{in}(A + \bar{A}) \\
 &= AB + ABC_{in} + A\bar{B}C_{in} + ABC_{in} + \bar{A}BC_{in} \\
 &= AB(1 + C_{in} + C_{in}) + A\bar{B}C_{in} + \bar{A}BC_{in} \\
 &= AB + A\bar{B}C_{in} + \bar{A}BC_{in} \\
 &= AB + C_{in}(A\bar{B} + \bar{A}B) \\
 &= AB + C_{in}(A \oplus B)
 \end{aligned}$$

$$A + A = A$$


$$1 + A = 1$$

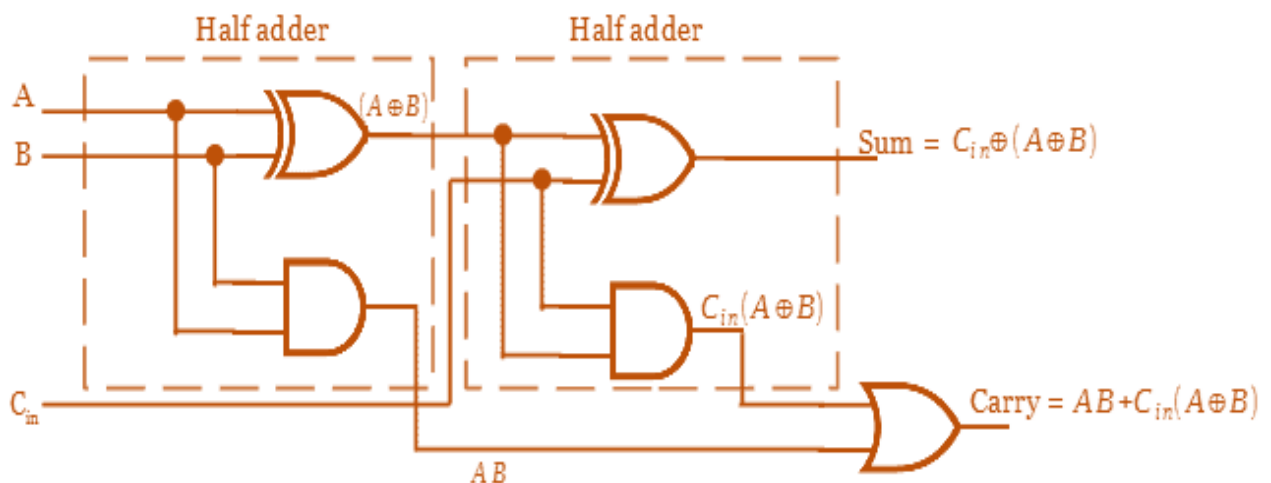


Realization of Full Adder with two half Adders (Picture is taken from: <https://www.electrically4u.com/half-adder-and-full-adder/>)



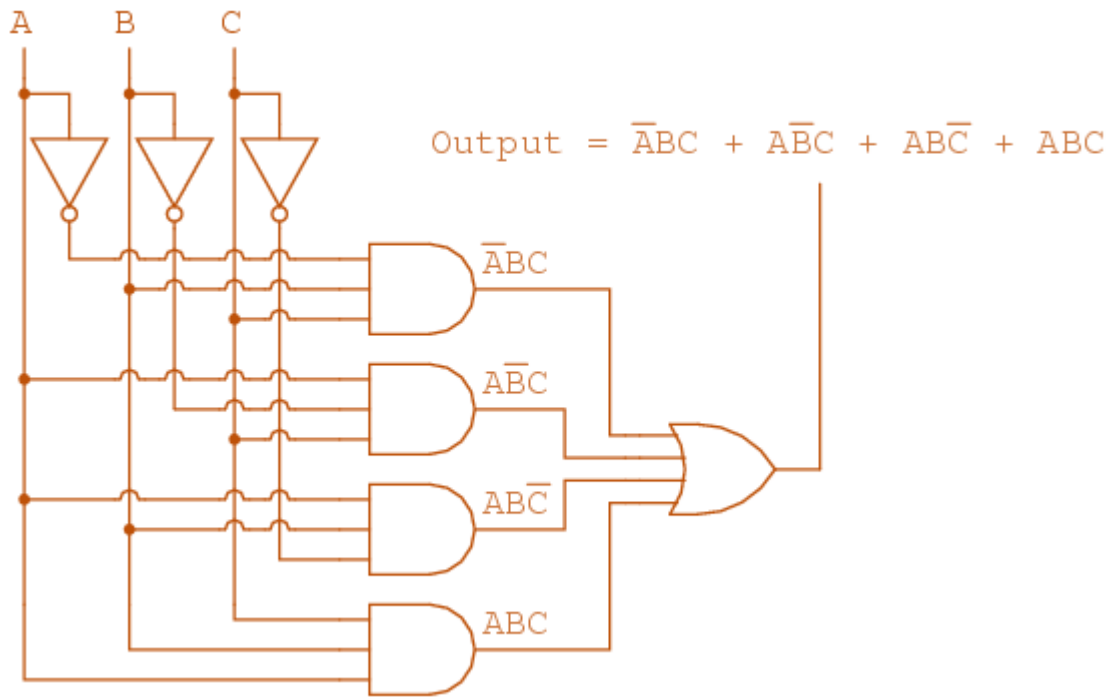COMPILED & CIRCULATED BY
Dr. Tapanendu Kamilya
Assistant Professor, Department of Physics, Narajole Raj College



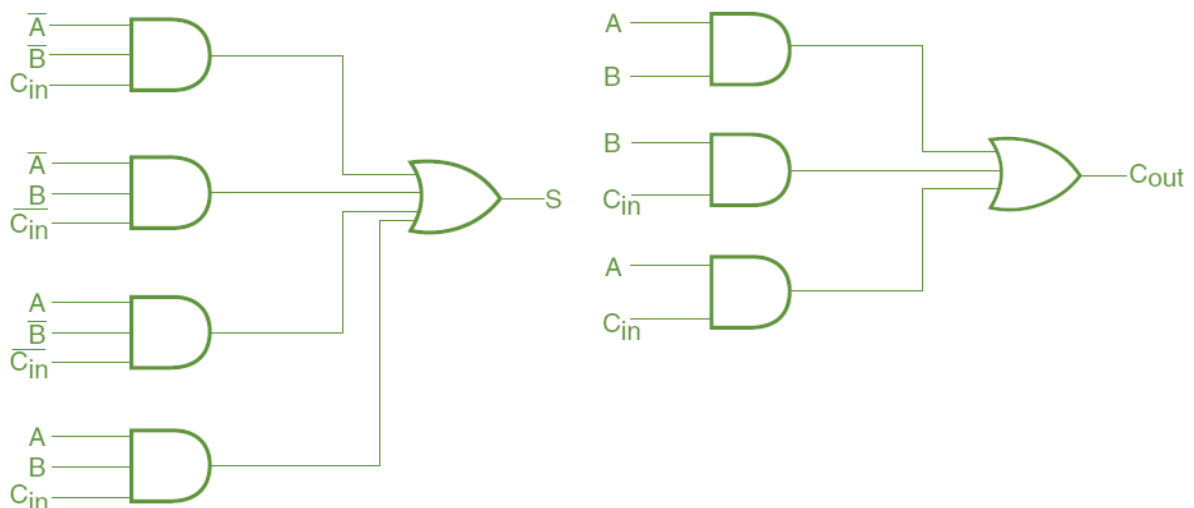
Circuit Diagram for SUM of Full Adder (Image source: https://www.ibiblio.org/kuphaldt/electricCircuits/Digital/DIG1_7.html)



Circuit Diagram for SUM and Carry of Full Adder



 COMPILED & CIRCULATED BY
Dr. Tapanendu Kamilya
Assistant Professor, Department of Physics, Narajole Raj College



Circuit Diagram for SUM and Carry of Full Adder by Basic Gates

References:

- (i) *Device Electronics for Integrated Circuits, 3rd Ed: R.S. Muller, T. I. Kamins, M. Chan, Published by WILEY (3rd Ed.).*
- (ii) *Fundamental Principles of Electronics, Author- B. Ghosh, Published by Books & Allied Pvt. Ltd. (2018 Ed.).*
- (iii) *Digital Integrated Circuits A Design Perspective- Author- J. M. Rabaey, A. Chandrakasan, B. Nolic, Published by PEARSON. (2nd Ed.).*
- (iv) <https://www.javaatpoint.com/addition-and-subtraction-using-2s-complement-in-digital-electronics>
- (v) <https://www.circuitstoday.com/half-adder>
- (vi) <https://www.ques10.com/p/32990/explain-full-adder-circuit-using-pla-having-three/>
- (vii) <https://www.electronics-tutorial.net/combinational-logic-circuits/full-adder/>
- (viii) <https://www.electrically4u.com/half-adder-and-full-adder/>
- (ix) https://www.ibiblio.org/kuphaldt/electricCircuits/Digital/DIGI_7.html



COMPILED & CIRCULATED BY

Dr. Tapanendu Kamilya

Assistant Professor, Department of Physics, Narajole Raj College

(x) http://www.edwardbosworth.com/My5155_Slides/Chapter05/FullAdder.htm

Here images from different sources are taken only for the preparation of class notes.

Link to Audio visual Lectures (e-Lectures) and NPTEL lectures on this topic given by Distinguish Professors of Indian & Foreign Universities:

- (1) <https://nptel.ac.in/content/storage2/courses/117106114/Week9%20Slides/9.3Adder.pdf>
- (2) <https://www.youtube.com/watch?v=KHgrJrcHr70>
- (3) <https://nptel.ac.in/courses/108/105/108105113/>
- (4) <https://nptel.ac.in/courses/117/105/117105080/>