




Prof. Surajit Dhara

SACT,

Dept. Of Physics, Narajole Raj College

C3T (Electricity and Magnetism) , Topic :- Electrical Circuits

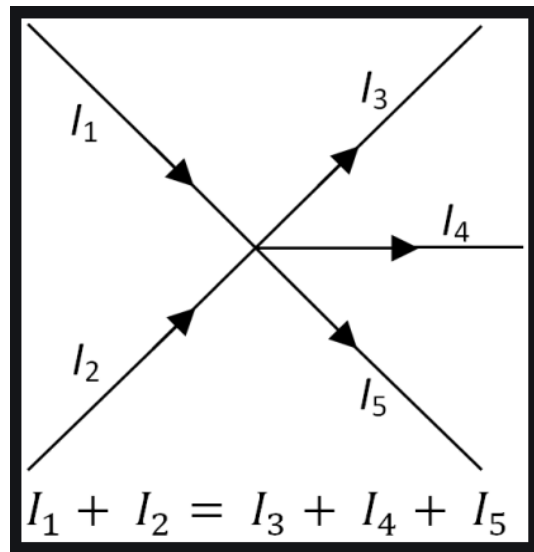- ❖ **Kirchhoff's Laws:** Kirchhoff's offered two laws which are applicable to complicated networks of conductor.
- **Kirchhoff's 1st Law:** The algebraic sum of currents meeting at a junction point of conductors is always zero.



- **Explanation:** Let i_1, i_2, i_3, \dots be the currents through conductors connected at a junction point. Then

$$i_1 + i_2 - i_3 + i_4 - i_5 = 0$$

i.e. $\boxed{\sum i = 0}$

- **Sign Convension:** The current towards the junction point = + Ve
The current outwards the junction point = -Ve

- **Proof :** From the equation of continuity,

$$\vec{\nabla} \cdot \vec{j} = -\frac{\partial \rho}{\partial t}$$

$$\Rightarrow \iiint \vec{\nabla} \cdot \vec{j} \, dv = -\iiint \frac{\partial \rho}{\partial t} \, dv$$


$$\Rightarrow \iiint \vec{j} \cdot \hat{n} \, ds = -\iiint \frac{\partial \rho}{\partial t} \, dv$$

$$\Rightarrow \boxed{\sum i = 0} \quad ; \text{ for steady current } \frac{\partial \rho}{\partial t} = 0$$

N.B- 1. Kirchhoff's 1st law being the law of conservation of electric charge.

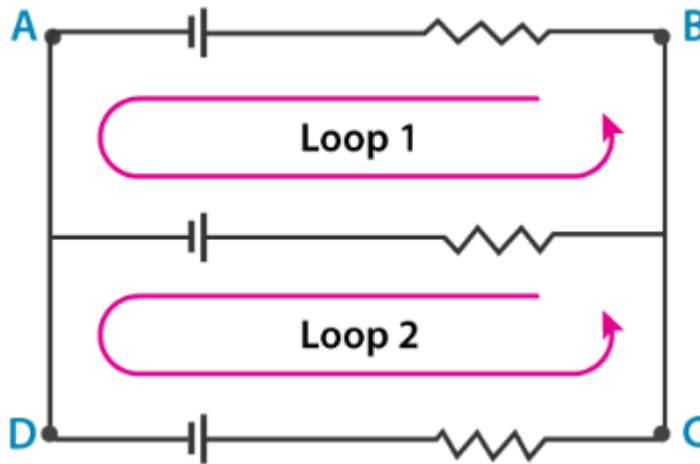2. It is known as Kirchhoff's current law or KCL

- **Kirchhoff's 2nd Law:** The algebraic sum of the product of current and resistance in each branch of a closed network of conductance is equal to the total emf in the circuit.




- Explanation : Let us take a closed loop ABCDEA, consisting branches having resistances r_1, r_2, r_3 , and e_1, e_2, e_3 . Then

$$\boxed{\sum ir = \sum e}$$

N.B – 1. 2nd law being the law of conservation of energy.

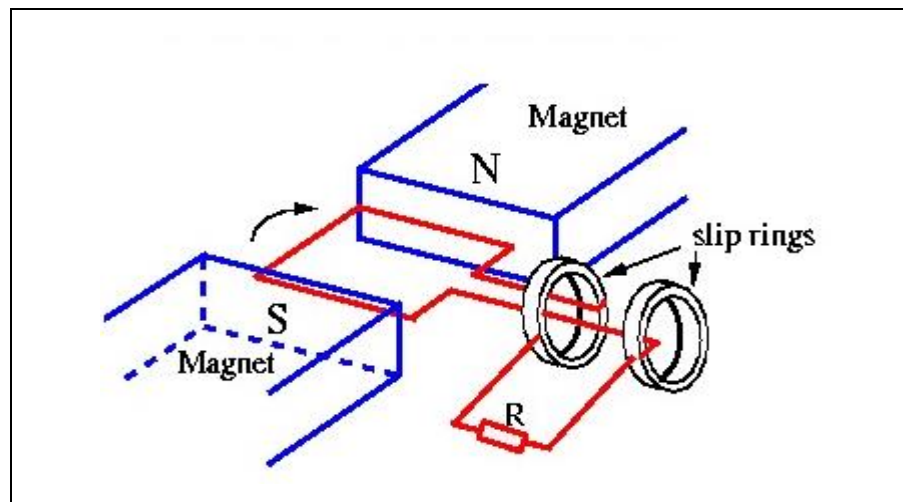2. It is called Kirchhoff's voltage law or KVL.

❖ **Production of Alternating Current:** Let at any moment the magnetic flux linked up with the coil,



$$\phi = N \int \vec{B} \cdot \hat{n} ds$$

Where N is the total no. of turns of the coil, B is the magnetic flux density, \hat{n} is the unit vector normal to the plane of the coil.

If θ be the angle between \vec{B} and \hat{n} , then

$$\phi = BAN \cos \theta \quad \dots(1)$$

If ω be the angular velocity then $\theta = \omega t$

$$\begin{aligned} \therefore \text{Induced emf } e &= -\frac{d\phi}{dt} \\ &= -\frac{d}{dt}(BAN \cos \omega t) \\ &= BAN \omega \sin \omega t \quad \dots(2) \end{aligned}$$

Where $BAN\omega = E_0$, the peak value of induced emf.

Thus the current passing through R,

$$i = \frac{E}{R} = \frac{E_0}{R} \sin \omega t$$

$$\Rightarrow i = i_0 \sin \omega t \quad \dots(3)$$

Where $i_0 = \frac{E_0}{R}$ the peak value of current.

❖ **Average Value of Alternating emf / current over Complete Cycle :** The instantaneous value of alternating emf

$$E = E_0 \sin \omega t \quad \dots(1) \text{ Taking imaginary part}$$

Thus average value of alternating emf. over complete cycle ,

$$\begin{aligned} E_{av} &= \frac{1}{T} \int_0^T E dt \\ &= \frac{1}{T} \int_0^T E_0 \sin \omega t dt \\ &= -\frac{E_0}{\omega T} [\cos \omega t]_0^T \\ &= -\frac{E_0}{2\pi} [\cos 2\pi - \cos 0] \quad \omega = \frac{2\pi}{T} \\ &= 0 \end{aligned}$$

Similarly, $i_{av} = 0$

❖ **Average Value of Alternating emf / current over Half Cycle :**

$$\begin{aligned} E_{av}|_{T/2} &= \frac{1}{T/2} \int_0^{T/2} E dt \\ &= \frac{2}{T} \int_0^{T/2} E_0 \sin \omega t dt \\ &= -\frac{iE_0}{\omega T} \left[\cos \frac{\omega T}{2} - \cos 0 \right] \\ &= \frac{2E_0}{\pi} \end{aligned}$$

Similarly, $i_{av}|_{T/2} = \frac{2i_0}{\pi}$

❖ **Root mean square (R.M.S) value of Alternating emf/current:-** The mean square value of alternating emf over a full cycle,

$$E_{m.s} = \frac{1}{T} \int_0^T E^2 dt$$

$$\begin{aligned}
&= \frac{1}{T} \int_0^T E^2 \sin^2 \omega t dt \\
&= \frac{E_0^2}{2T} \int_0^T (1 - \cos 2\omega t) dt \\
&= \frac{E_0^2}{2}
\end{aligned}$$

Thus root mean square (r.m.s) value of alternating emf,

$$E_{r.m.s} = \frac{E_0}{\sqrt{2}}$$

Similarly,
$$i_{r.m.s} = \frac{i_0}{\sqrt{2}}$$

➤ **Form Factor :** The ratio of r.m.s value of alternating emf. to the average value (over half cycle) is known as form factor.

$$\therefore \text{Form factor } F = \frac{E_{r.m.s}}{E_{av}} = \frac{\pi}{2\sqrt{2}} = 1.11$$

$$F = 1.11$$

➤ **Average Power calculation:** Average power for a complete cycle of alternating current, average power,

$$\begin{aligned}
P_{av} &= \frac{1}{T} \int_0^T E_0 i_0 \sin^2 \omega t dt = \frac{E_0 i_0}{T} \times \frac{T}{2} \\
&= \frac{E_0}{\sqrt{2}} \times \frac{i_0}{\sqrt{2}}
\end{aligned}$$

$$\therefore P_{av} = E_{r.m.s} \times i_{r.m.s}$$