




Prof. Surajit Dhara

SACT,

Dept. Of Physics, Narajole Raj College

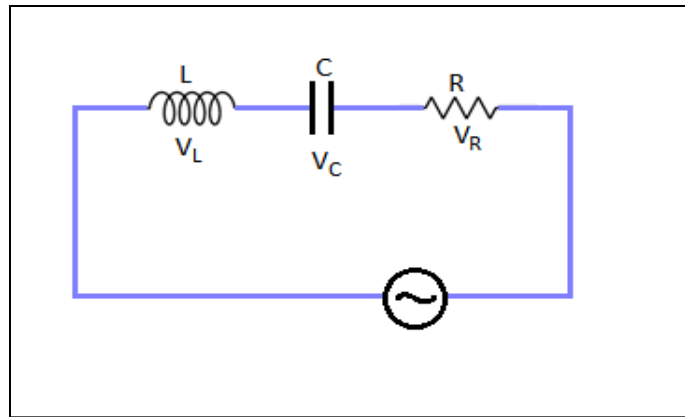**C3T ( Electricity and Magnetism) , Topic :- Electrical Circuits**

❖ **Sinusoidal Voltage Applied to a Series L-C-R Circuit:** Let us consider an alternating emf.  $E(t) = E_0 e^{j\omega t}$  is applied in a circuit containing a resistance R, an inductance L and a capacitance C in series.



Let  $q(t)$  be the charge through the capacitor at any instant  $t$  and instantaneous current is  $i$ , where  $i = \frac{dq}{dt}$ . So the instantaneous voltage,

Across the resistance =  $Ri$

Across the inductance =  $-L \frac{di}{dt}$

Across the capacitance =  $q/c$

Thus KVL equation for the circuit,

$$Ri + \frac{q}{c} = E(t) - L \frac{di}{dt}$$
$$\Rightarrow \boxed{Ri + L \frac{di}{dt} + \frac{1}{c} \int i dt = E_0 e^{j\omega t}} \quad \dots(1)$$

➤ Solution:- Let  $i(t) = Ae^{j\omega t}$  be the trial solution. From the equation (1)

$$RAe^{j\omega t} + LAj\omega e^{j\omega t} + \frac{A}{i\omega c} e^{j\omega t} = E_0 e^{i\omega t}$$

$$\Rightarrow A \left( R + j\omega L + \frac{1}{j\omega c} \right) = E_0$$

$$\Rightarrow A = \frac{E_0}{R + j(\omega L - \frac{1}{\omega c})} \quad \dots\dots(2)$$

Thus the current in the circuit,

$$i(t) = \frac{E_0 e^{j\omega t}}{R + j(\omega L - \frac{1}{\omega c})}$$

$$= \frac{R - j(\omega L - \frac{1}{\omega c})}{R^2 + (\omega L - \frac{1}{\omega c})^2} \cdot E_0 e^{j\omega t}$$

$$= \frac{E_0}{\sqrt{(R^2 + (\omega L - \frac{1}{\omega c})^2)}} \left[ \frac{R}{\sqrt{(R^2 + (\omega L - \frac{1}{\omega c})^2)}} - j \frac{(\omega L - \frac{1}{\omega c})}{\sqrt{(R^2 + (\omega L - \frac{1}{\omega c})^2)}} \right] e^{j\omega t}$$

$$\text{Put, } \frac{R}{\sqrt{(R^2 + (\omega L - \frac{1}{\omega c})^2)}} = \cos\theta$$

$$\frac{(\omega L - \frac{1}{\omega c})}{\sqrt{(R^2 + (\omega L - \frac{1}{\omega c})^2)}} = \sin\theta$$

$$\therefore \tan\theta = \frac{\omega L - \frac{1}{\omega c}}{R}$$

$$\therefore i = \frac{E_0}{\sqrt{(R^2 + (\omega L - \frac{1}{\omega c})^2)}} e^{-j\theta} \cdot e^{j\omega t}$$

$$\Rightarrow \boxed{i = i_0 e^{j(\omega t - \theta)}}$$

$$\text{Where } i_0 = \frac{E_0}{\sqrt{(R^2 + (\omega L - \frac{1}{\omega c})^2)}}$$

$$i = i_0 [\cos(\omega t - \theta) + j \sin(\omega t - \theta)]$$

$i_0 \cos(\omega t - \theta) \Rightarrow$  Real part of current

$i_0 \sin(\omega t - \theta) \Rightarrow$  Imaginary part of current

➤ **Peak Value of Current:**

$$i_0 = \frac{E}{|Z|} = \frac{E_0}{\sqrt{(R^2 + (\omega L - \frac{1}{\omega c})^2)}}$$

➤ **Impedance:**  $z = \frac{E}{i} = R + j(\omega L - \frac{1}{\omega c})$

$$\vec{Z} = \vec{R} + j(\omega \vec{L} - \frac{1}{\omega c})$$

$$|Z| = \sqrt{(R^2 + (\omega L - \frac{1}{\omega c})^2)}$$


Inductive reactance  $X_L = \omega L$

Capacitive reactance  $X_c = \frac{1}{\omega c}$

➤ Impedance diagram and phasor diagram:-

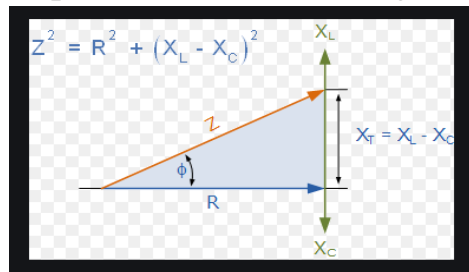
a) When  $\omega L > \frac{1}{\omega c}$  i.e. inductive reactance is greater than capacitive reactance. Here

$\phi$  is positive; which implies that the current lags behind the emf by an angle  $\phi$



$$\text{where } \phi = \tan^{-1} \frac{\omega L - \frac{1}{\omega c}}{R}$$

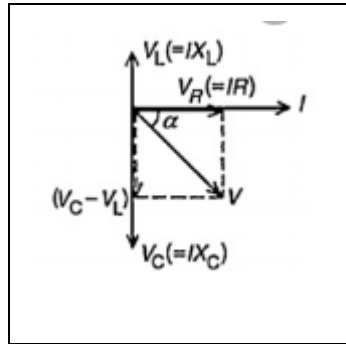
b) When  $\frac{1}{\omega c} > \omega L$  i.e. when capacitive reactance is greater than inductive reactance.



Here  $\alpha = -Ve$ ; which implies that the current leads the applied emf by an angle

$$\alpha = \tan^{-1} \left( \frac{\frac{1}{\omega c} - \omega L}{R} \right)$$

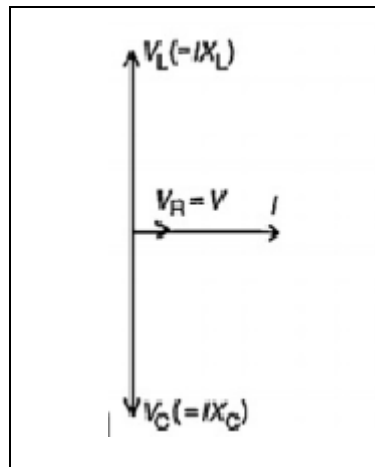c) When  $\omega L = \frac{1}{\omega c}$  i.e when inductive reactance is equal to capacitive reactance.




Here  $\theta = 0$  i.e the circuit is purely resistive.

➤ **Series Resonant Circuit:** The circuit containing inductor(L), capacitor(c) and resistor(R) are connected in series and subjected to an alternating emf. Where

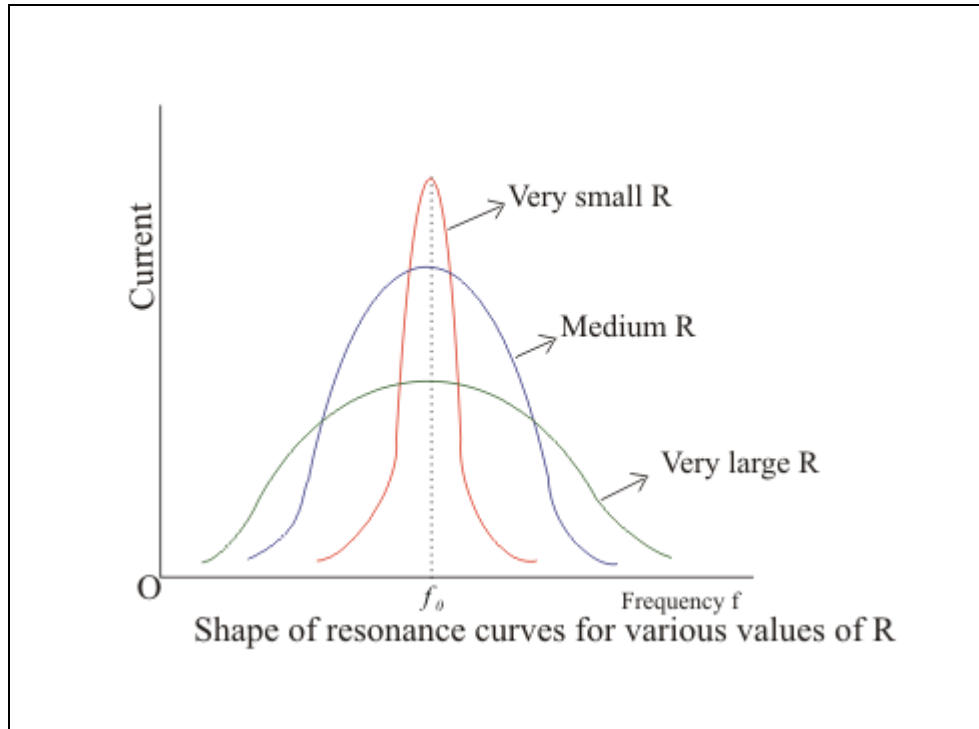- (i) The circuit behaves as purely resistive.
- (ii) Impedance is minimum.
- (iii) Current is maximum
- (iv) The emf and current will be in same phase.

Then the circuit is called series resonant circuit.

- **Sharpness of Resonance of a Series L-C-R Circuit:** For a series L-C-R circuit the maximum current  $i_0 = \frac{E_0}{\sqrt{(R^2 + (\omega L - \frac{1}{\omega c})^2)}}$ ; At resonance,  $\omega L = \frac{1}{\omega c}$  then  $i_0 = \frac{E_0}{R}$




The curves plotting the current versus frequency ( $f$  and  $\omega$ ) are known as resonance curves. From the figure we see that when the resistance in the circuit is reduced the resonance curve become sharper. The peak value of  $i$  shows that, the circuit responds only to the frequency exactly equal to the natural frequency of the circuit  $\omega_0 = \frac{1}{\sqrt{LC}}$ . This resonance is sharp. The sharpness of resonance is a measure of the rate of fall of amplitude from its maximum value at resonance frequency on either side of it.

- **Quality Factor:** Sharpness of resonance curve is determined by quality factor, called “Q” of the circuit. Which is defined as the ratio of the reactance ( $X_L$  or  $X_C$ ) to the impedance at resonant frequency is called Quality factor of the circuit. i.e.

$$Q = \frac{X_L}{Z} \Big|_{\omega_0} = \frac{\omega_0 L}{R}$$

$$\text{Or, } Q = \frac{X_C}{Z} \Big|_{\omega_0} = \frac{1}{\omega_0 c R}$$

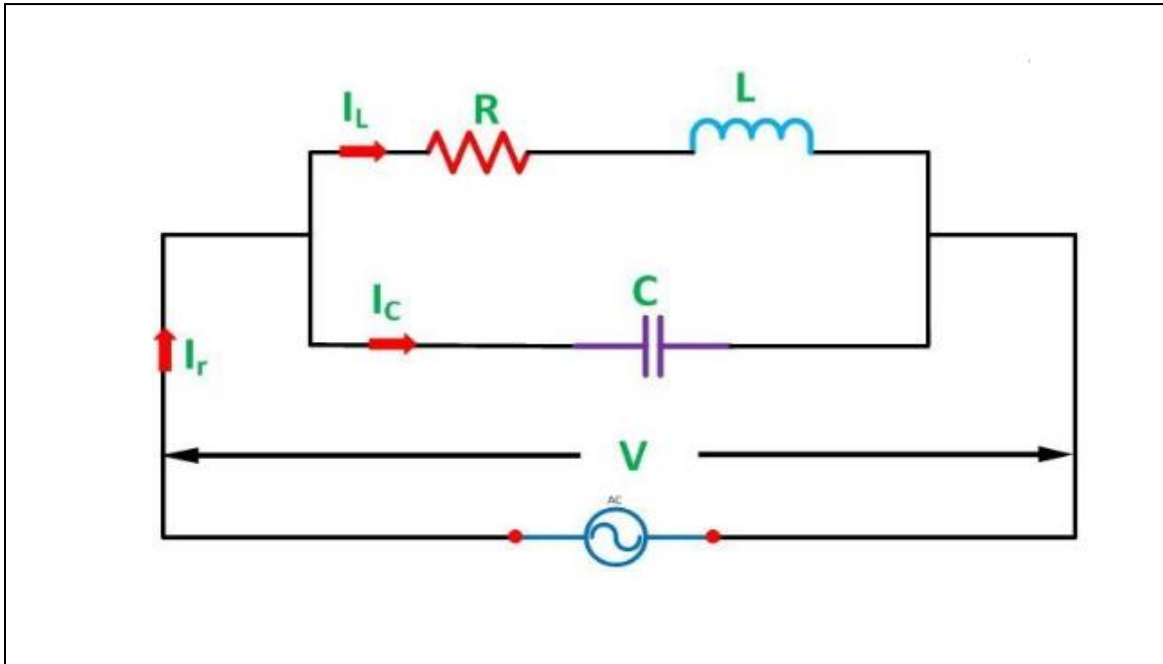❖ **Parallel L-C-R Circuit:** Let the combination is connected to alternating emf,  $E = E_0 e^{j\omega t}$ . If  $Z$  be the total impedance for the combination then,



$$\frac{1}{Z} = \frac{1}{Z_{L-R}} + \frac{1}{Z_c}$$

$$\Rightarrow \frac{1}{Z} = \frac{1}{R + j\omega L} + j\omega c$$

$$\Rightarrow z = \frac{R + j\omega L}{(1 - \omega^2 LC) + j(\omega c R)}$$

$$= \frac{R + j\omega L}{(1 - \omega^2 LC) + j(\omega c R)} \times \frac{(1 - \omega^2 LC) - j(\omega c R)}{(1 - \omega^2 LC) - j(\omega c R)}$$

$$\therefore z = \frac{R + j[\omega L - \omega c(\omega^2 L^2 + R^2)]}{(1 - \omega^2 LC)^2 + \omega^2 c^2 R^2}$$

$$= \frac{R}{(1 - \omega^2 LC)^2 + \omega^2 c^2 R^2} + j\omega \frac{L - c(\omega^2 L^2 + R^2)}{(1 - \omega^2 LC)^2 + \omega^2 c^2 R^2}$$

$$= R_0 + j\omega L_0 \text{ (say)}$$

Where  $R_0 = \frac{R}{(1-\omega^2 LC)^2 + \omega^2 c^2 R^2}$ ; effective resistance of the coil.

$L_0 = \frac{L - c(\omega^2 L^2 + R^2)}{(1-\omega^2 LC)^2 + \omega^2 c^2 R^2}$ ; effective inductance of the coil.

➤ **Magnitude of Impedance:-**

$$|z| = \sqrt{R_0^2 + \omega^2 L_0^2}$$

$$|z| = \left[ \frac{R^2 + \omega^2 L^2}{(1 - \omega^2 LC)^2 + \omega^2 c^2 R^2} \right]^{1/2}$$

➤ **Resonant Frequency :-** The parallel at which the circuit is purely resistive or current will be in same phase with the emf is known as resonant frequency. At  $\omega = \omega_0$ ,  $L_0 = 0$

$$\Rightarrow L - c(\omega_0^2 L^2 + R^2) = 0$$

$$\Rightarrow \omega_0^2 L^2 + R^2 = 0$$

$$\Rightarrow \omega_0^2 L^2 = \frac{L}{c} - R^2$$

$$\Rightarrow \omega_0^2 = \frac{1}{Lc} - \frac{R^2}{L^2}$$

$$\Rightarrow \omega_0 = \sqrt{\frac{1}{Lc} - \frac{R^2}{L^2}}$$

Parallel resonant frequency,

$$f_0 = \frac{1}{2\pi} \sqrt{\frac{1}{Lc} - \frac{R^2}{L^2}}$$

➤ **Condition of Parallel Resonance:** For parallel resonance,  $\omega_0 = \text{real}$  (must)

$$\Rightarrow \sqrt{\frac{1}{Lc} - \frac{R^2}{L^2}} > 0$$

$$\Rightarrow \frac{1}{Lc} - \frac{R^2}{L^2} > 0$$

$$\Rightarrow R^2 < \frac{L}{c}$$

$$\Rightarrow R < \sqrt{\frac{L}{c}}$$

Hence for parallel resonance resistance R should be kept as low as possible.